
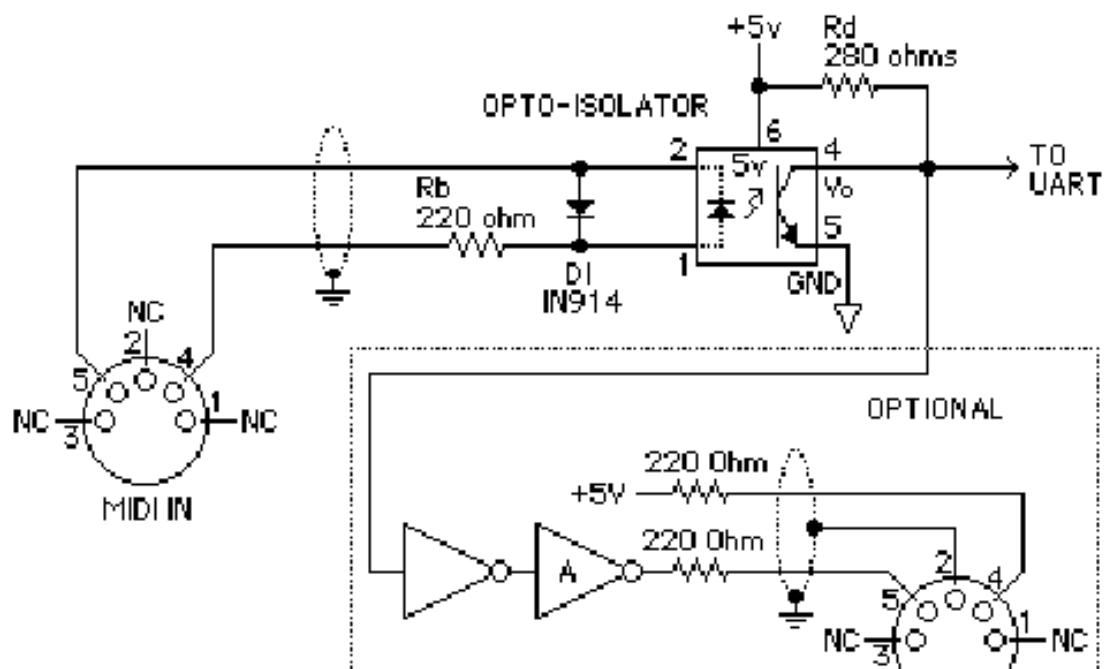


MIDI Electrical Specification Diagram & Proper Design of Joystick/MIDI Ada

Figure 1: Electrical Specification Diagram

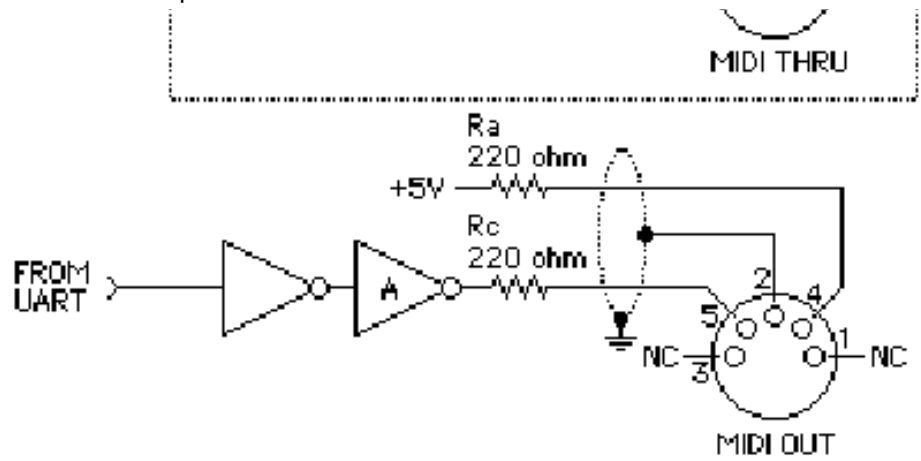



Copyright 1985 MIDI Manufacturers Association


MIDI Standard Hardware NOTES:


1. Opto-isolator shown is Sharp PC-900. HP 6N138 or other can be used with changes.
2. Gates "A" are IC or transistor; Resistors are 5%.
3. Maximum cable length is fifty feet (15 meters), terminated on each end by a 5-pin DIN male plug (i.e. 05GM5M).
4. Cable is shielded twisted pair, with shield connected to pin 2 at both ends.

Figure 2: Joystick/MIDI Adapter Diagram

(Note: Clicking on the Image will open a full size Image in a new Wind

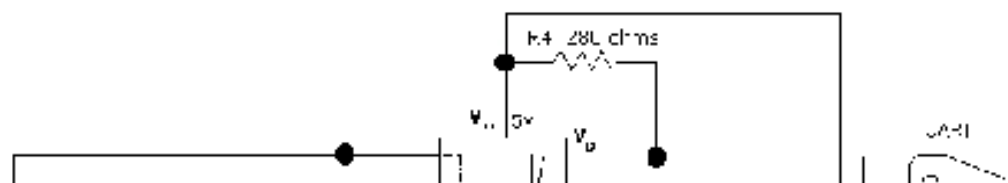Computer Sound Card 4-pin Port to Standard MIDI Connector



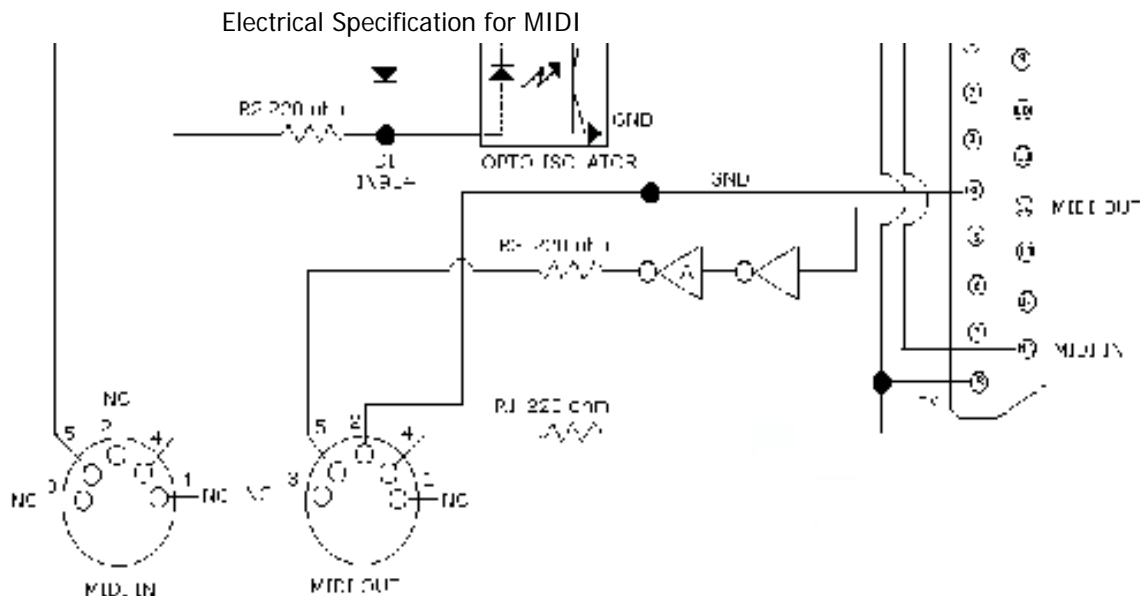

Joystick Adapter NOTES:

1. A good choice for the Optoisolator 6N137. A 6N138 will work, but is slower.
2. Resistors are 5%
3. Inverter A can be an IC or a transistor.
4. It is extremely important not to ground pin 2 of the MIDI IN connector. A noise-causing ground loop will do. Pin 2 of the MIDI OUT connector should be grounded. That way the shield of the MIDI cable will be grounded as desired.

Ground loops will cause horrendous hum, buzzes, and other noises, especially when connected to computer lighting equipment. The noises are caused by differences in voltage potential from one end of the cable to the other. The remedy, of course, is to run balanced audio lines and to NEVER physically connect the chassis grounds of different pieces of equipment together. MIDI instrument designers understand ground loops. In fact, a major design goal in the electrical specification explanation in the MIDI Specification Document, is to prevent any ground to occur with the MIDI cables. This is done by using a balanced current loop through an opto-isolator and on MIDI outputs. The MIDI IN connector is not grounded to the receiver's chassis. When done correctly, there are no ground loops and no hum or other noises caused by the MIDI setup.

All materials, graphics, and text copyright © 1995-2010 MIDI Manufacturers Association Incorporated. Use is prohibited without written permission.

Designers of personal computers are not generally audio engineers and apparently have not heard of ground loops. Given the noisy fans and screaming disk drives that go into the PC, it is a wonder they can hear at all. All some audio professionals keep the computer in a closet or another room. But the primary source of ground loops in PC audio is the PC soundcard MIDI interface.

A PC soundcard exports the serial MIDI signal from its UART on two pins of its joystick or game port. A cable connects this to the approved MIDI connector, and is supposed to include the necessary opto-isolator for converting the unbalanced signal to a balanced current loop. The MIDI IN connector is supposed to have the opto-isolator and no ground connection to the shield for the express purpose of avoiding a ground loop.

We were able to locate six different such cables, all of which violate the MIDI hardware specification by grounding pin 2 of the MIDI connectors (MIDI IN and MIDI OUT). ALL of these cables will cause ground loops, and generate hum and unnecessary noise.